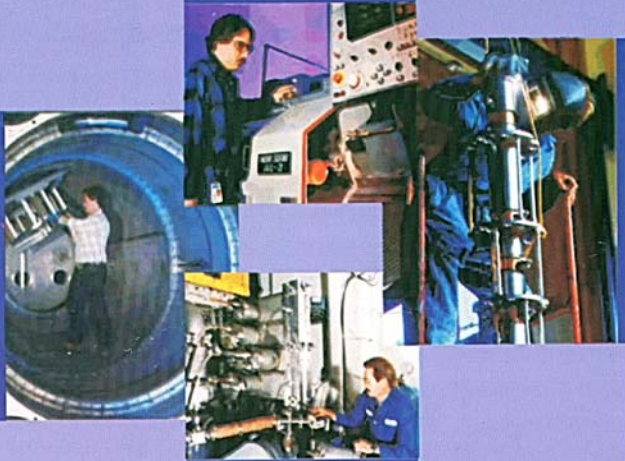


Principles of Electrical and Electronics Engineering



Jaspreet Singh Dhillon
Jarnail Singh Dhillon
Diljinder Singh

PRINCIPLES OF ELECTRICAL & ELECTRONICS ENGINEERING

Jaspreet S. Dhillon,
Jarnail S. Dhillon
Diljinder Singh

1. Basics of Electricity

1-54

- 1.1 History
 - 1.2 Modern Electron
 - 1.3 Current
 - 1.3.1 Alternating Current and Direct current
 - 1.4 Current Density
 - 1.5 Voltage
 - 1.5.1 A.C. and D.C. voltage
 - 1.6 E.M.F.
 - 1.7 Potential Difference
 - 1.8 Electric energy
 - 1.9 Electric power
 - 1.10 Resistance
 - 1.10.1 Resistivity
 - 1.10.2 Effect of temperature on resistance
 - 1.10.3 Energy lost in resistance
 - 1.10.4 Resistor
 - 1.11 Conductance
 - 1.11.1 Conductance
 - 1.11.2 Conductor
 - 1.11.3 Semiconductor
 - 1.11.4 Insulator
 - 1.11.5 Superconductor
 - 1.12 Capacitance
 - 1.12.1 Electric Field
 - 1.12.2 Charging and Discharging of a Capacitor
 - 1.12.3 Energy stored in capacitor
 - 1.12.4 Capacitors in parallel
 - 1.12.6 Types of Capacitors
 - 1.13 Inductance
 - 1.13.1 Magnetic Field
 - 1.13.2 Magnetic Flux
 - 1.13.3 Flux Density
 - 1.13.4 Electromagnetism
 - 1.13.5 Magneto-motive Force and Magnetic Field Strength
 - 1.13.6 Reluctance
 - 1.13.7 Permeability
 - 1.13.8 Self Inductance
 - 1.13.9 Energy stored in inductor
 - 1.13.10 Mutual Inductance
 - 1.13.11 Dot Notation
 - 1.13.12 Types of Inductors
 - 1.14 Concept of electric current
 - 1.15 Concept of magnetic circuit
 - 1.16 Comparison between magnetic and electric current
 - 1.17 Ideal Source
 - 1.18 Source transformation
- Additional solved examples*
Summary of formulae

	<i>Objective questions</i>	
	<i>Short answer questions</i>	
	<i>Questions</i>	
	<i>Problems</i>	
2.	<i>Electric Circuits</i>	55-94
2.1	Terminology of circuit	
2.2	Ohm's law	
2.3	Open circuit and short circuit	
2.4	Kirchhoff's Law	
	2.4.1 Kirchhoff's Current Law	
	2.4.2 Kirchhoff's Voltage Law	
2.5	Combination of resistors	
	2.5.1 In series	
	2.5.2 In parallel	
	2.5.3 Star Connection	
	2.5.3 Delta Connection	
	2.5.4 Delta to Star conversion	
	2.5.5 Star to Delta conversion	
2.6	Current division	
2.7	Voltage division	
2.8	Wheat stone bridge	
2.9	Mesh analysis	
2.10	Nodal analysis	
2.11	Measurement of current, voltage and resistance	
2.12	Protective devices	
	<i>Additional solved examples</i>	
	<i>Summary of formulae</i>	
	<i>Objective questions</i>	
	<i>Short answer questions</i>	
	<i>Questions</i>	
	<i>Problems</i>	
3.	<i>Basic Laws of Electric and Magnetic Circuits</i>	95-110
3.1	Coulomb's Law	
3.2	Biot-savart's Law	
3.3	Ampere's Law	
3.4	Faraday's Law	
3.5	Lenz's Law	
3.6	Fleming's Left hand rule	
3.7	Fleming's right hand rule	
3.8	Gauss's Law	
3.9	Ampere's Circuital Law	
	<i>Additional solved examples</i>	
	<i>Summary of formulae</i>	
	<i>Objective questions</i>	
	<i>Short answer questions</i>	
	<i>Questions</i>	
	<i>Problems</i>	
4.	<i>A.C. Sinusoidal Current & Voltage</i>	111-192
4.1	Introduction	
4.2	Angular Displacement	
4.3	Relation between degree and radian	
4.4	Angular velocity	
4.5	A projection during uniform circular motion of phasor	

- 4.6 Production of alternating voltage
- 4.7 Expression of the alternating voltage
- 4.8 Representation of sinusoidal voltage & current equation
- 4.9 A C Supply
- 4.10 Phasor
 - 4.10.1 Phasor representation
 - 4.10.2 Two phasor with phase difference
- 4.11 Euler's formula
- 4.12 Complex numbers and complex algebra
 - 4.12.1 Conversion from exponential to polar form
 - 4.12.2 Conversion from rectangular to polar form
 - 4.12.3 Conversion from polar to rectangular form
 - 4.12.4 Conjugate of a complex number
- 4.13 Periodic functions
- 4.14 Average value
- 4.15 Root Mean square value
- 4.16 Average value of sine wave
- 4.17 Root Mean square value of sine wave
- 4.18 Resistance
 - 4.18.1 A.C. through resistor
 - 4.18.2 Power dissipated in a resistor
 - 4.18.3 Equivalent resistance
- 4.19 Capacitance
 - 4.19.1 A.C. through capacitor
 - 4.19.2 Power through capacitor
 - 4.19.3 Energy stored in a capacitor
 - 4.19.4 Equivalent capacitance
- 4.20 Inductance
 - 4.20.1 A.C. through Inductor
 - 4.20.2 Power through Inductor
 - 4.20.3 Energy stored in a Inductor
 - 4.20.4 Equivalent Inductance
- 4.21 Admittance
 - 4.21.1 ZY conversion
- 4.22 R-L series circuit
- 4.23 R-C series circuit
- 4.24 R-L-C series circuit
- 4.25 Real power
- 4.26 Reactive power
- 4.27 Apparent power
- 4.28 Comparison of various types of power absorbed by circuit elements/combinations
- 4.29 Complex power
- 4.30 Series resonance
- 4.31 Voltage and current in Series Resonant Circuit
- 4.32 Band Width of R-L-C- circuit
- 4.33 Quality Factor
- 4.34 Magnification of Resonance
- 4.35 A.C. parallel circuit
- 4.36 Resonance in parallel circuit
- 4.37 Resonant frequency for tank circuit
- 4.38 Variation of impedance with frequency
- 4.39 Q-factor of parallel resonance

4.40	Comparison of series and parallel resonance <i>Additional solved examples</i> <i>Summary of formulae</i> <i>Objective questions</i> <i>Short answer questions</i> <i>Questions</i> <i>Problems</i>	
5.	<i>Network Theorems</i>	193-231
5.1	Mesh Analysis	
5.2	Node Analysis	
5.3	Thevenin Theorem	
5.4	Norton Theorem	
5.5	Super-position Theorem	
5.6	Maximum Power Transfer Theorem	
5.7	Reciprocity Theorem	
5.8	Millman's Theorem <i>Additional solved examples</i> <i>Summary of formulae</i> <i>Objective questions</i> <i>Short answer questions</i> <i>Questions</i> <i>Problems</i>	
6.	<i>Three Phase system</i>	232-254
6.1	Introduction	
6.2	Interconnection of the Three phases	
6.3	Current and Voltage relations for star connection	
6.4	Current and Voltage relations for delta connection	
6.5	Power in three phase system	
6.6	Star-delta equivalence	
6.7	Measurement of three phase power	
6.7.1	One wattmeter method	
6.7.2	Two wattmeter method of measuring three phase power	
6.7.3	Two wattmeter method for balanced load to calculate power factor	
	<i>Additional solved examples</i> <i>Summary of formulae</i> <i>Objective questions</i> <i>Short answer questions</i> <i>Questions</i> <i>Problems</i>	
7.	<i>Magnetic Circuits</i>	255-281
7.1	Introduction	
7.2	Magnetic Circuits	
7.3	Simple Magnetic Circuit	
7.4	Series Magnetic Circuit	
7.5	Parallel Magnetic Circuit	
7.6	Leakage Flux	
7.7	Comparison between Magnetic and Electric Circuit	
7.8	Magnetic Effect of Electric Current	
7.9	Current carrying conductor in Magnetic Field	
7.10	Law of Electromagnetic Induction	
7.10.1	Statement of Faraday's Law	
7.10.2	Lenz's Law	

- 7.10.3 Fleming's Right Hand Rule
- 7.11 Induced EMF
 - 7.11.1 Dynamically Induced EMF
 - 7.11.2 Statically Induced EMF
 - i) Self Induced EMF
 - ii) Mutually Induced EMF
- 7.12 Self Inductance
 - 7.12.1 Definition
 - 7.12.2 Equation of Self Inductance
 - 7.12.3 Relationship between self induced emf & self inductance
- 7.13 Mutual Inductance
 - 7.13.1 Definition
 - 7.13.2 Equation of Mutual Inductance
 - 7.13.3 Relation between mutual inductance & mutually induced emf
- 7.14 Coupling coefficient between two magnetically coupled circuits
 - Additional solved examples*
 - Summary of formulae*
 - Objective questions*
 - Short answer questions*
 - Questions*
 - Problems*

8. Electrical Machines

282-395

- 8.1 Transformer
 - 8.1.1 Introduction
 - 8.1.2 Working principle of Transformer
 - 8.1.3 Construction
 - 8.1.4 Types of Transformers
 - 8.1.5 EMF equation of transformer
 - 8.1.6 Transformation ratio
 - 8.1.7 Transformer with No-magnetic leakage
 - 8.1.8 An Ideal Transformer
 - 8.1.9 Equivalent circuit of a transformer on No-Load
 - 8.1.10 Leakage Flux and Leakage Reactance
 - 8.1.11 Equivalent Circuit of a Transformer
 - 8.1.12 Approximate Equivalent Circuit
 - 8.1.13 Phasor Diagram of a Transformer On-Load
 - 8.1.14 Losses and Efficiency of a Transformer
 - 8.1.15 Condition for Maximum Efficiency
 - 8.1.16 All Day Efficiency
 - 8.1.17 Voltage Regulation for a Transformer
 - 8.1.18 Testing of Transformer
 - 8.1.19 Auto Transformer
 - 8.1.20 Instrument Transformer
 - 8.1.21 Cooling of Transformers
 - 8.1.22 Three Phase Transformer
- 8.2 D.C. Generator
 - 8.2.1 Introduction
 - 8.2.2 Construction
 - 8.2.3 Armature Winding
 - 8.2.4 Working Principle of DC Generator
 - 8.2.5 Generated EMF in DC Generator
 - 8.2.6 Armature Reaction
 - 8.2.7 Commutation

- 8.2.8 Types of DC Generators
 - 8.2.9 Electrical equivalent circuit DC Generators
 - 8.2.10 Characteristics of DC Generators
 - 8.2.11 Voltage Regulation
 - 8.2.12 Application of DC Generators
 - 8.3 D.C. Motor
 - 8.3.1 Construction
 - 8.3.2 Principle of operation
 - 8.3.3 Back EMF
 - 8.3.4 Equivalent Circuit of DC Motors
 - 8.3.5 Torque and Speed Equations
 - 8.3.6 Factors Affecting Speed of DC Motor
 - 8.3.7 Speed Control Method
 - 8.3.8 DC Motor Starter
 - 8.3.9 Application of DC Motors
 - 8.4 Three Phase Induction Motor
 - 8.4.1 Introduction
 - 8.4.2 Construction
 - 8.4.3 Revolving Magnetic Field
 - 8.4.4 Principle Operation of 3-Phase Induction Motors
 - 8.4.5 Slip
 - 8.4.6 Frequency of Rotor EMF
 - 8.4.7 Induction Motor versus Transformer
 - 8.4.8 Induced Rotor EMF and Rotor Circuit
 - 8.4.9 Equivalent Circuit of Induction Motor
 - 8.4.10 Losses in induction motor
 - 8.4.11 Relation Between Slip and Rotor I²R loss
 - 8.4.12 Torque
 - 8.4.13 Torque-Slip Characteristics
 - 8.4.14 Starting of Induction Motor
 - 8.4.15 Starters used for Induction Motor
 - 8.4.16 Application of Induction Motors
- Additional solved examples*
Summary of formulae
Objective questions
Short answer questions
Questions
Problems

9. Measuring Instruments

396-411

- 9.1 Introduction
- 9.2 Classification of Instruments
- 9.3 Basic Principles of Indicating Instruments
 - 9.3.1 Deflecting Torque
 - 9.3.2 Controlling Torque
- 9.4 Moving Iron Instruments
 - 9.4.1 Attraction type- Moving Iron Instruments
 - 9.4.2 Repulsion type-Moving Iron Instruments
- 9.5 Moving Coil Instruments
 - 9.5.1 Permanent Magnet Moving Coil Type
 - 9.5.2 Dynamometer Type
- 9.6 Induction Type
 - 9.6.1 Energy Meter
- 9.7 Megger

Additional solved examples
Summary of formulae
Objective questions
Short answer questions
Questions
Problems

10. Transducers

412-428

- 10.1 Introduction
- 10.2 Capacitive Transducer
- 10.3 Inductive Transducer
- 10.4 Linear Variable Differential Transformer (LVDT)
- 10.5 Potentiometric Transducer
- 10.6 Electrical Strain Gauges
 - 10.6.1 Unbonded Strain Gauge
 - 10.6.2 Bonded Wire Strain Gauge
- 10.7 Thermistor
- 10.8 Thermocouple
- 10.9 Hall Effect
- 10.10 Piezo Electric Transducer
- 10.11 Photo-electric Transducer
- 10.12 Resistance Thermometer

Additional solved examples
Summary of formulae
Objective questions
Short answer questions
Questions
Problems

11. Semi Conductor Devices

429-501

- 11.1 Atomic Structure of Semi-Conductors
- 11.2 Atomic Bonding
- 11.3 Conduction in Semi-Conduction Materials
- 11.4 N-type and P-Type Semi –Conductors
- 11.5 PN Junction
- 11.6 Biasing the Diode
- 11.7 Diode Characteristics
- 11.8 Half Wave Rectifiers
- 11.9 Full Wave Rectifiers
- 11.10 Rectifier filters
- 11.11 Diode Clipping and Clamping Circuits
- 11.12 Zener Diodes
- 11.13 Bipolar Junctions Transistors (BJTs)
- 11.14 Configurations and characteristics of Transistor
- 11.15 Field Effect Transistor (FET)
- 11.16 JFET Characteristics
- 11.17 Comparison of JFER and BJT
- 11.18 Metal Oxide Semiconductor Field Effect Transistor (MOSFET)
- 11.19 Uni-Junction Transistor (UJT)
- 11.20 Thyristors
 - 11.20.1 Silicon Controlled Rectifiers (SCRs)
 - 11.20.2 Triac
 - 11.20.3 Diac
- 11.21 Opto-Electronic Devices
 - 11.21.1 Photoconductive cell

- 11.21.2 Photo Voltaic Cell
 - 11.21.3 Solar Cell
 - 11.21.4 Photo Tube
 - 11.21.5 Photo Multiplier
 - 11.21.6 Photo diode
 - 11.21.7 Photo Transistor
 - 11.22 Display Devices
 - 11.22.1 Light Emitting Diode (LED)
 - 11.22.2 Infra Red (IR) Emitters
 - 11.22.3 Liquid Crystal Display (LCD)
 - 11.22.4 Nixie tube
 - 11.22.5 Alphanumeric Displays
 - 11.22.6 Opto-coupler
 - 11.22.7 Cathode Ray Tube (CRT)
- Additional solved examples*
Summary of formulae
Objective questions
Short answer questions
Questions
Problems

12. Integrated Circuits

502-528

- 12.1 Introduction
 - 12.2 Manufacturing process of Monolithic IC's
 - 12.3 Formation of Diode
 - 12.4 Formation of Resistor
 - 12.5 Formation of Capacitor
 - 12.6 Advantages and disadvantages of Integrated Circuits
 - 12.7 Operational Amplifier
 - 12.8 Circuit symbol and packages
 - 12.9 Ideal Operational Amplifier
 - 12.10 Applications
 - 12.10.1 Inverting amplifier
 - 12.10.2 Non-inverting amplifier
 - 12.10.3 Sign changer
 - 12.10.4 Scale Changer
 - 12.10.5 Summing amplifier
 - 12.10.6 Differentiator
 - 12.10.7 Integrator
- Additional solved examples*
Summary of formulae
Objective questions
Short answer questions
Questions
Problems

13. Digital Electronics

529-612

- 13.1 Digital system and Signals
- 13.2 Decimal Number System
 - 13.2.1 Compliment form
- Binary Number System
- 13.3
 - 13.3.1 Binary to decimal conversion
 - 13.3.2 Decimal to binary conversion
 - 13.3.3 Binary arithmetic operation
 - 13.3.4 1's Complement

- 13.3.5 2's Complement
- 13.3.6 Subtraction using complement
- 13.6.7 Binary Multiplication
- 13.6.8 Binary Division
- 13.4 Octal Number System
 - 13.4.1 Octal to binary conversion
 - 13.4.2 Binary to octal conversion
 - 13.4.3 Octal to decimal conversion
 - 13.4.4 Decimal to octal conversion
- 13.5 Hexadecimal Number System
 - 13.5.1 Hexadecimal to binary conversion
 - 13.5.2 Binary to hexadecimal conversion
 - 13.5.3 Hexadecimal to octal conversion
 - 13.5.4 Octal to hexadecimal conversion
 - 13.5.5 Hexadecimal to decimal conversion
 - 13.5.6 Decimal to Hexadecimal conversion
- 13.6 Binary Codes
 - 13.6.1 BCD code
 - 13.6.2 Excess-3 code
 - 13.6.3 Gray Code
 - 13.6.4 Alphanumeric code
 - 13.6.5 Error detection code
- 13.7 Logic Gates
 - 13.7.1 AND gate
 - 13.7.2 OR gate
 - 13.7.3 NOT gate
 - 13.7.4 NAND gate
 - 13.7.5 NOR gate
 - 13.7.6 Exclusive-OR gate
 - 13.7.7 Exclusive –NOR gate
 - 13.7.8 Pulsed operation of Logic gates
 - 13.7.9 Boolean algebra based on truth tables
- 13.8 Flip-Flops
 - 13.8.1 S-R flip-flop
 - 13.8.2 D flip-flop
 - 13.8.3 J-K flip-flop
 - 13.8.4 T flip-flop
 - 13.8.5 Flip-flop operating characteristics
 - 13.8.6 Conversion of flip-flop

Additional solved examples

Summary of formulae

Objective questions

Short answer questions

Questions

Problems

Appendix A

Appendix B

Bibliography

613

614

615-616